

Experiment-1

P.No 1

Verification of Thevenin's Theorem

Aim:-

To simulate the given circuit using Mat lab Simulink & Verify Thevenin's theorem.

Apparatus Required:-


1. Laptop/Desktop
2. MATLAB

Requirements:-


Components	Tool Box/Library browser	Block	Parameters
Voltage Source	Simpower systems/ Electrical Sources	DC Voltage Source	Amplitude = 50V, 40V
Resistors	Simpower systems/ Elements	Series RLC Branch (Select R)	Resistance (Ohm) = 10, 40, 12, 30 & 20
Measurements	Simpower Systems/ Electrical Measurements	Current/ Voltage Measurement	Default
Display Powergui	Simulink/ Simsce Simpower systems/ Elements	Display Powergui	Default Continuous

Theoretical Calculations:-

CKT-1:

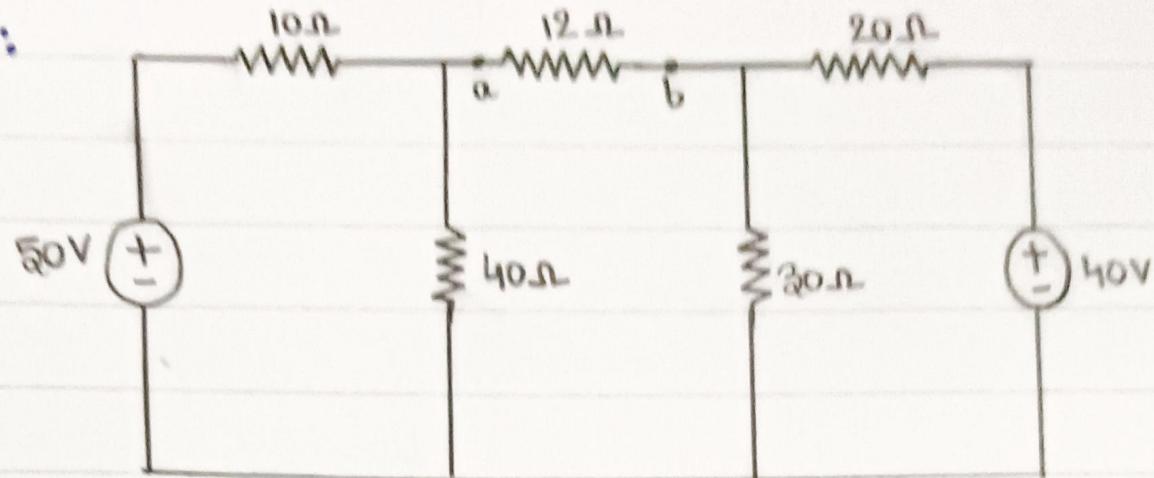

CKT-2: To find V_{th}

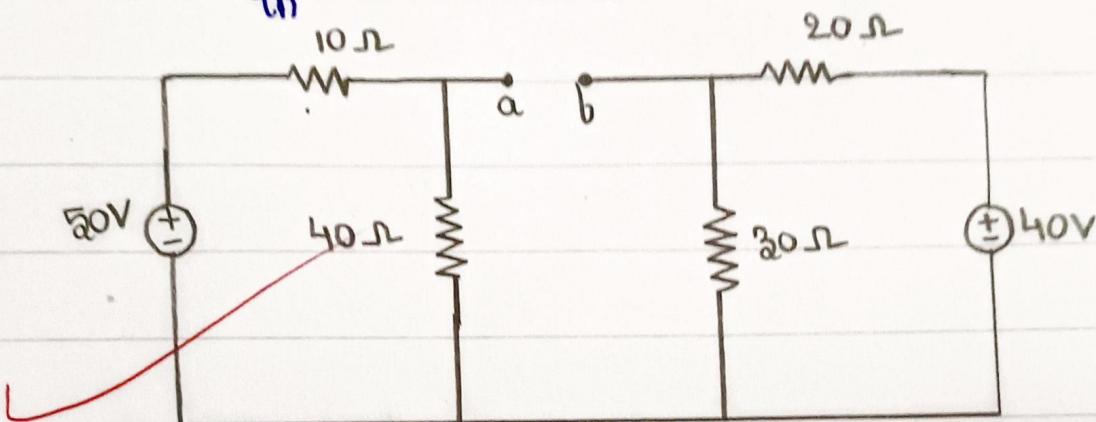

$$V_a = 50 \times \frac{40}{40+10}$$

$$V_a = 40 \text{ V}$$


$$V_b = 40 \times \frac{30}{30+20}$$

$$V_b = 40 \times \frac{30}{50}$$


$$V_b = 24 \text{ V}$$

$$\therefore V_{ab} = V_a - V_b \\ V_{ab} = 40 - 24 \\ V_{ab} = 16V \\ V_{ab} = V_{Th} = 16V$$

Ckt-3 : To find R_{Th} :-

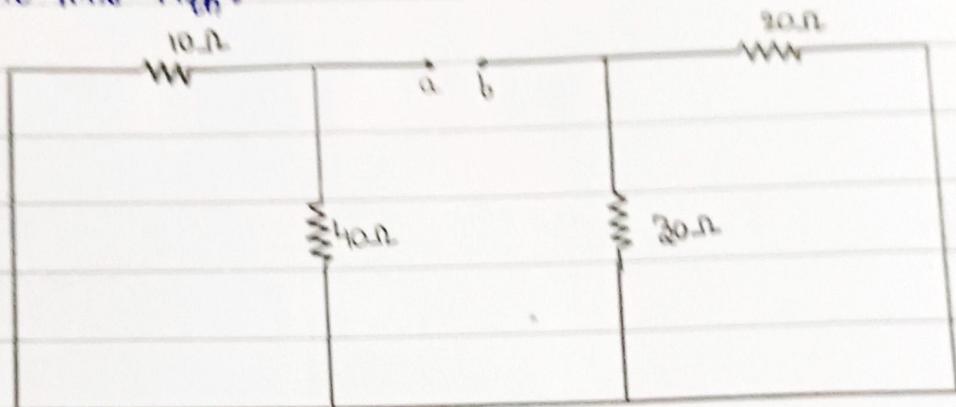

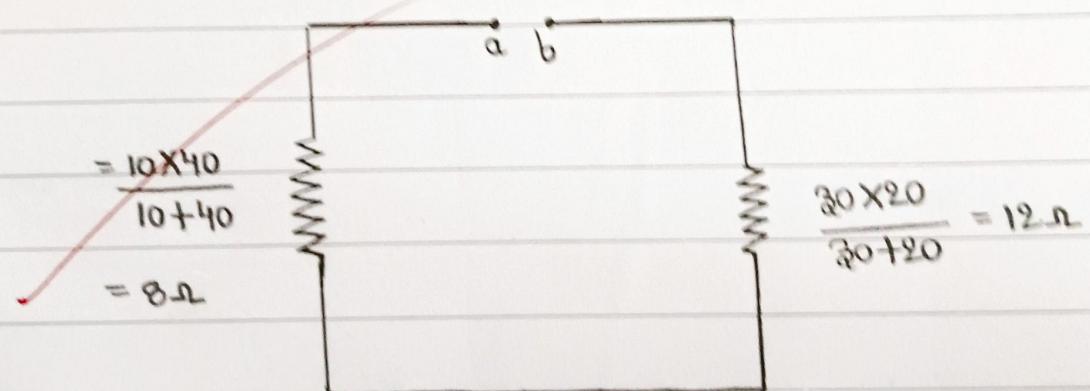
The above circuit can be redrawn as follows



$$R_{Th} = 8\Omega + 12\Omega$$

$$\therefore R_{Th} = 20\Omega$$

Ckt-4: Equivalent Thevenin circuit

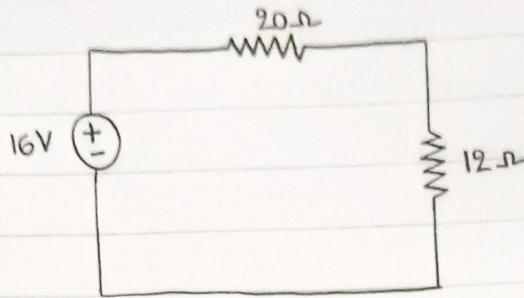

We get the Equivalent values as follows

$$V_{th} = 16V$$

$$R_{th} = 20\Omega$$

\therefore Voltage across 12Ω resistor is

$$V_{12\Omega} = V_{th} \times \frac{R_L}{R_L + R_{th}}$$

$$V_{12\Omega} = 16 \times \frac{12}{12 + 20}$$


$V_{12\Omega} = 6V$

Comparison Table:-

Q.No	Parameter	Theoretical	Practical
1.	V_{th}	16V	16V
2.	R_{th}	20Ω	20Ω
3.	$V_{12\Omega}$	6V	6V

Result:-

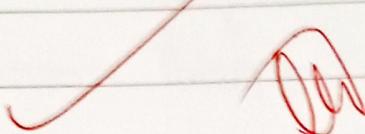Hence Thevenin's Theorem is verified both theoretically as well as using Simulation tools.



DR
19/01/2011

Experiment - 2

P.No 7

Verification of Norton's Theorem

Aim:

To simulate the given circuit using Mat lab Simulink & verify Norton's Theorem.

Apparatus Required:


1. Laptop / Desktop
2. MATLAB

Requirements:


Components	Tool Box/ Library browser	Block	Parameters
Voltage source	Simpower Systems/ Electrical sources	DC voltage source	Amplitude = $\frac{1}{2}0V, 40V$
Resistors	Simpower Systems/ Elements	Series RLC Branch (Select R)	Resistance (Ohm) $=10, 40, 12, 30$ & 20
Measurements	Simpower Systems/ Electrical Measure -ments	Current/ Voltage Measurement	Default
Display Powergui	Simulink/Simins Simpower Systems/ elements	Display Display powergui	Default Default Continuous

Theoretical Calculations:-

CKT-1

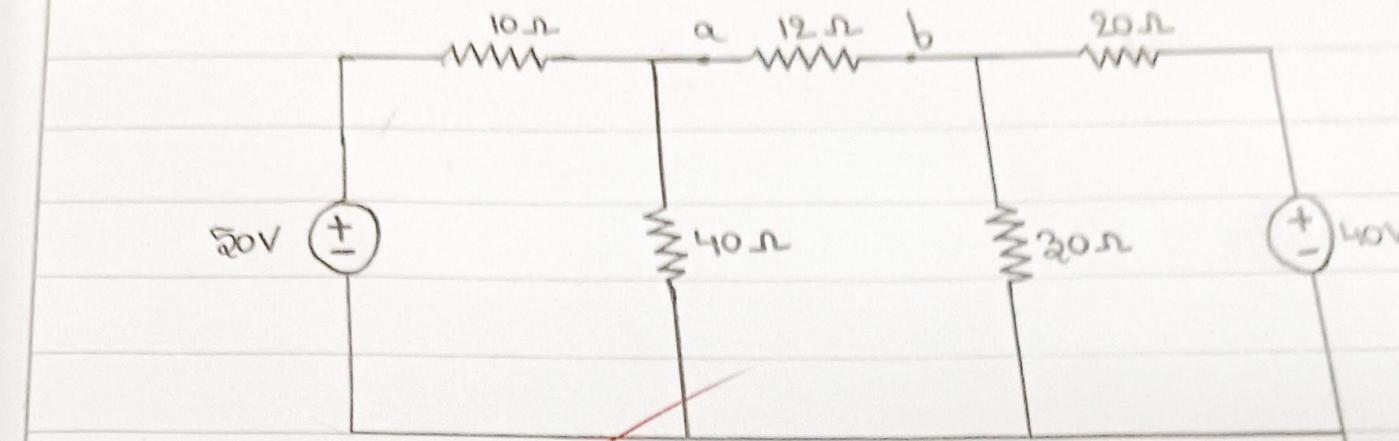

CKT-2: 1

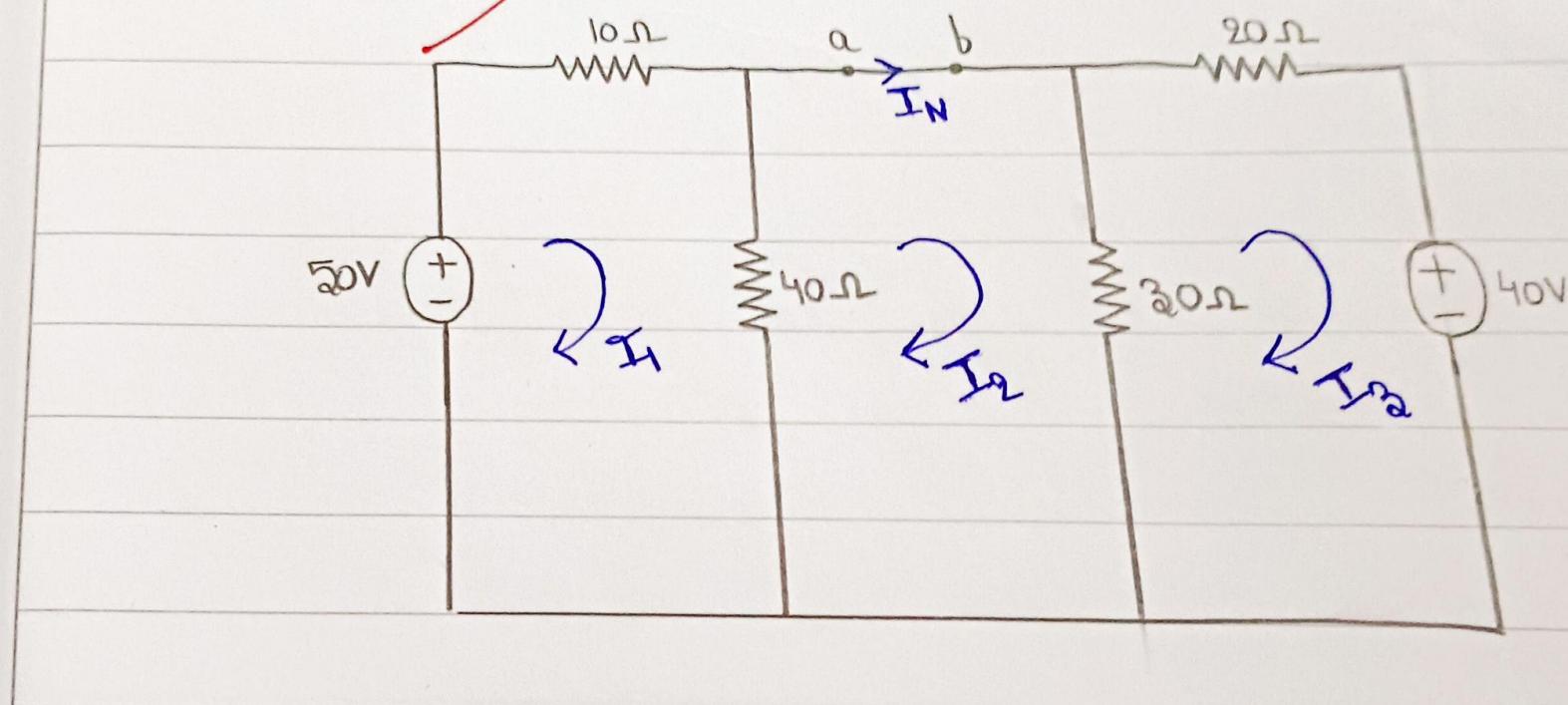

$$20 - 10(I_1) - 40(I_2 - I_3) = 0$$

$$-20I_1 + 40I_2 = -20 \quad \text{--- (1)}$$

$$-40(I_2 - I_3) - 30(I_3 - I_2) = 0$$

$$-40I_2 + 30I_3 + 40I_2 - 30I_3 = 0$$

$$-10I_2 + 40I_3 = 0 \quad \text{--- (2)}$$

$$-20I_3 - 40 - 30(I_3 - I_2) = 0$$

$$-50I_3 + 30I_2 = 20 \quad \text{--- (3)}$$


Adding eq (1) & (2) & (3)

We get $I_1 = 1.64$


$$I_2 = 0.8$$

$$I_3 = 0.32$$

Circuit :-

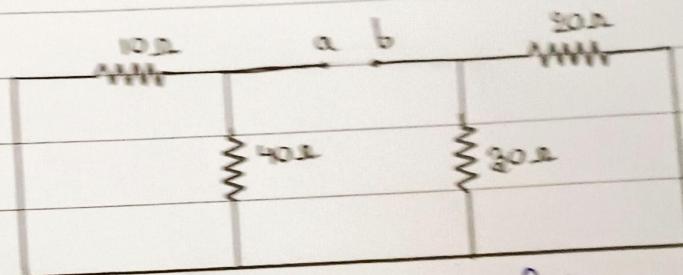


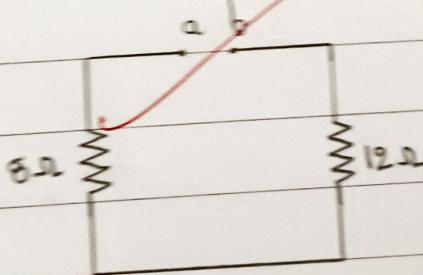The above circuit can be redrawn as follows



$$R_{ab} = 8 + 12 = 20 \Omega$$

Ckt-4: Equivalent circuit

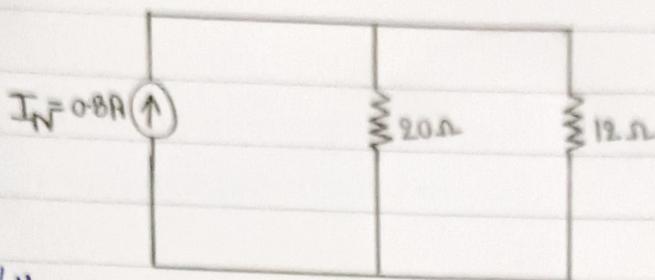

Voltage across 12Ω

$$0.8 = \frac{V_{ab}}{20} + \frac{V_{ab}}{12}$$

$$V_{ab} = 6V$$

Compassision Table:

Q.No	Parameters	Theoretical	Practical
1.	I	0.8A	0.8A
2.	R_N	20Ω	20Ω
3.	$V_{12\Omega}$	6V	6V

Result: Hence Norton's theorem is verified both theoretically as well as using Simulation tools.

26/11/2021

Experiment - 3

P No 19

Verification of Superposition Theorem

Aim:

To simulate the given circuit using Mat lab Simulink & verify superposition theorem.

Apparatus Required:


1. Laptop / Desktop
2. MATLAB

Requirements:

Components	Tool Box / Library SimPower Systems / Electrical Sources	Block DC Voltage Source	Parameters Amplitude = 50V, 40V
Resistors	SimPower Systems / Elements	Series RLC Branch (Select R)	Resistance (Ohm) = 10, 40, 12, 30 & 20.
Measurements	SimPower Systems / Electrical Measurements	Current / Voltage Measurement	Default
Display Powergui	SimPower Systems / Elements	Display Powergui	Default Continuous

Theoretical Calculations:-

C.R.T :-

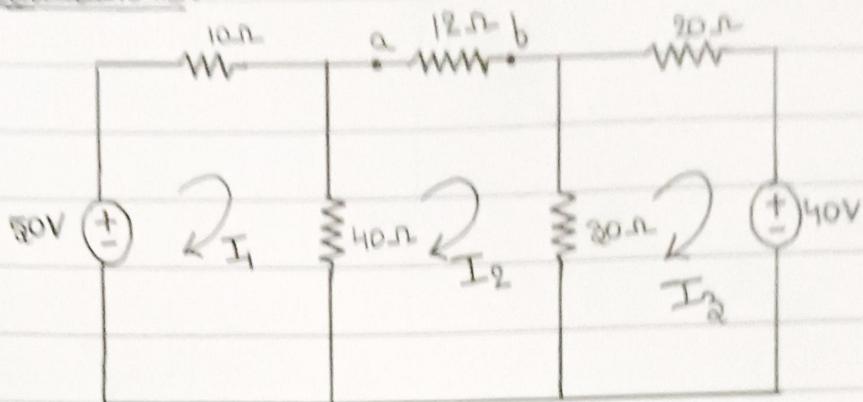

$$-50 + 10I_1 + 40(I_1 - I_2) = 0$$

$$50I_1 - 40I_2 = 50 \quad \text{--- (1)}$$

$$-40(I_2 - I_1) + 12I_2 + 30(I_3 - I_2) = 0$$

$$-30I_1 + 82I_2 + 30I_3 + 40I_1 = 0$$

$$82I_2 - 40I_1 + 30I_3 = 0 \quad \text{--- (2)}$$

$$20I_3 + 30(I_3 - I_2) = 0$$

$$-30I_2 + 50I_3 = 0 \quad \text{--- (3)}$$

$$I_1 = 2A$$

$$I_2 = 1.25A$$


$$I_3 = 0.75A$$

$$V_{ab} = 1.25 \times 12$$

$$V_{ab} = 15V$$

By solving ① & ② & ③, we get

Ckt-3:-

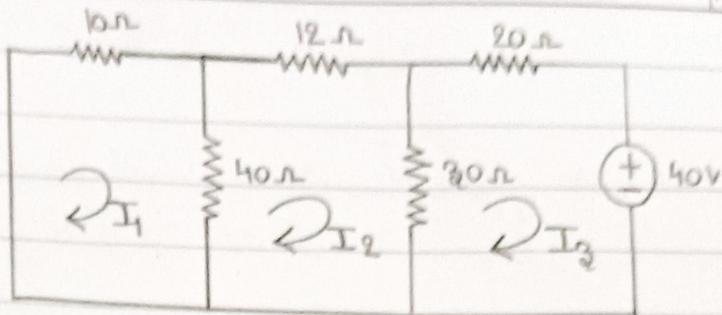

$$10I_1 + 40(I_1 - I_2) = 0 \quad \text{---} \textcircled{1}$$

$$-40(I_2 - I_1) + 12I_2 + 30(I_2 - I_3) = 0$$

$$-40I_2 + 42I_2 + 40I_1 - 30I_3 = 0$$

$$2I_2 + 40I_1 - 30I_3 = 0 \quad \text{---} \textcircled{2}$$

$$-30(I_3 - I_2) + 20I_3 + 40 = 0$$

$$I_1 = -0.6A$$

$$I_2 = -0.75A$$

$$I_3 = -1.25A$$

$$V_{ab_2} = -0.75 \times 12$$

$$V_{ab_2} = -9V$$

$$V_{ab_1} + V_{ab_2} = V_{ab}$$

$$15 + (-9) = V_{ab}$$

$$\boxed{V_{ab} = 6V}$$

(Ans)
03/12/2021

Composition Table:-

S.N.O	Parameter	Theoretical	Practical
1.	V_{ab_1}	15V	15V
2.	V_{ab_2}	-9V	-9V
3.	V_{ab}	6V	6V

Result:- Hence Superposition theorem is verified both theoretically as well as using Simulation tools.

Experiment-4

P.No 16

Verification of KCL & KVL

Aim: To simulate the given circuit using MATLAB Simulink
& Verify KCL & KVL


Apparatus Required:

1. Laptop / Desktop
2. MATLAB

Requirements

Components	Tool Box/ Library browser	Block	Parameters
Voltage Source	Simpower systems/ Electrical Sources	DC Voltage Source	Amplitude = 50V, 40V
Resistors	Simpower systems/ Elements	Series RLC Branch (Select R)	Resistance (ohm) = 10, 40, 12, 30 & 20
Measurements	Simpower Systems / Electrical Measurements	Current/ Voltage Measurement	Default
Display Powergui	Simulink/Sinks Simpower systems/ Elements	Display Powergui	Default Continuous

Theoretical Calculation for KCL :-

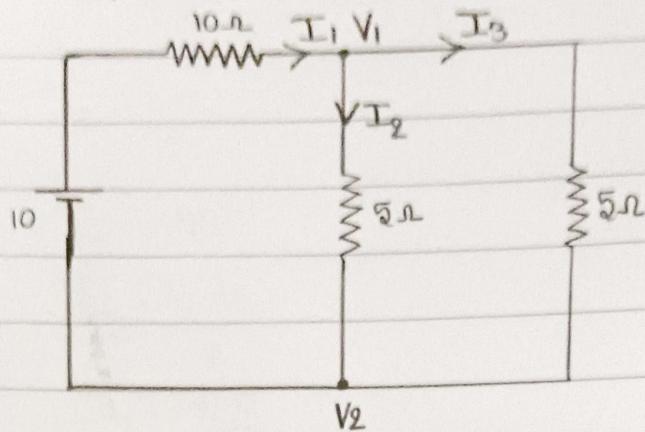

$$I_1 = I_2 + I_3$$

$$\frac{V_2 - V_1 + 10}{10} = \frac{V_1 - V_2}{2} + \frac{V_1 - V_2}{5}$$

$$\frac{0 - V_1 + 10}{10} = \frac{V_1 - 0}{2} + \frac{V_1 - 0}{5}$$

$$\frac{-V_1}{10} + 1 = \frac{V_1}{5} + \frac{V_1}{5}$$

$$1 = \frac{2V_1}{5} + \frac{V_1}{10}$$

$$1 = \frac{4V_1 + V_1}{10}$$

$$10 = 5V_1$$

$$V_1 = 2V$$

$$I_1 = \frac{V_2 - V_1 + 10}{10}$$

$$I_1 = \frac{0 - 2 + 10}{10}$$

$$I_1 = 0.8A$$

$$I_2 = \frac{V_1 - V_2}{5}$$

$$I_2 = \frac{2-0}{5}$$

$$I_2 = 0.4\text{A}$$

$$I_3 = \frac{V_1 - V_2}{8}$$

$$I_3 = \frac{2-0}{8}$$

$$I_3 = 0.4\text{A}$$

$$I_1 = I_2 + I_3$$

$$0.8 = 0.4 + 0.4$$


$$0.8 = 0.8$$

Hence KCL is verified theoretically

Compassion Table:-

Q.No	Parameters	Theoretical	Practical
1.	I_1	1.875A	1.875A
2.	$I_2 = I_N$	0.625A	0.625A
3.	I_3	1.25A	1.25A

Theoretical Calculation:-

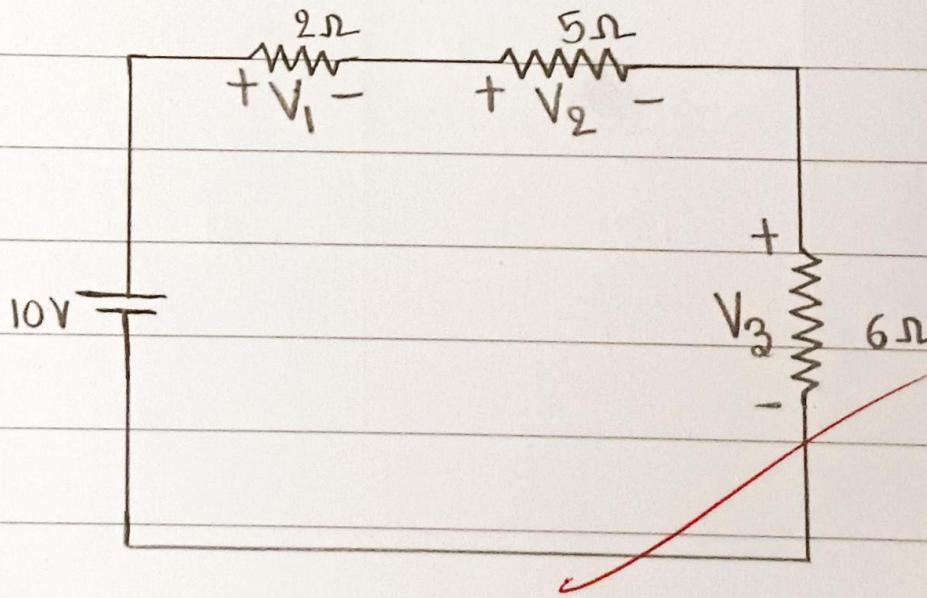

$$-10 + V_1 + V_2 + V_3 = 0$$

$$-10 + 2I + 5I + 6I = 0$$

$$-10 + 13I = 0$$

$$I = \frac{10}{13}$$

$$I = 0.769$$

$$V_1 = IR$$

$$V_1 = 0.769 \times 2$$

$$V_1 = 1.538$$

$$V_2 = 5 \times 0.769 = 3.845V$$

$$V_3 = 6 \times 0.769 = 4.614V$$

$$-10 + 1.538 + 3.845 + 4.614 = 0$$

$$9.997 = 10$$

$$10 = 10$$

Comparison Table:-

S. No	Parameters	Theoretical	Practical
1.	V_1	2V	2V
2.	V_2	4V	4V
3.	V_3	4V	4V

Result:-

Hence KCL & KVL is verified both theoretically as well as using simulation tools.

Dr
10/12/2021

Verification of mesh analysis

Aims:

To simulate the given circuit using MATLAB Simulink and verify Mesh analysis.


Apparatus Required :-

1. Laptop/Desktop
2. MATLAB

Requirements :-

Components	Tool box/ Library browser Simpower system /electrical sources Simpower system/ Elements	Block DC voltage source Series RLC branch (Select R)	Parameters Amplitude = 50V, 40V Resistance (R) = 10, 40, 12, 30 8 ohm
Voltage Source			
Resistors			
Measurements	Simpower systems /electrical measurement	Current/ Voltage measurement	Default
Display Powergui	Simulink/Sinks Simpower system /Elements	Display Powergui	Default Continuous

Theoretical Calculations:-

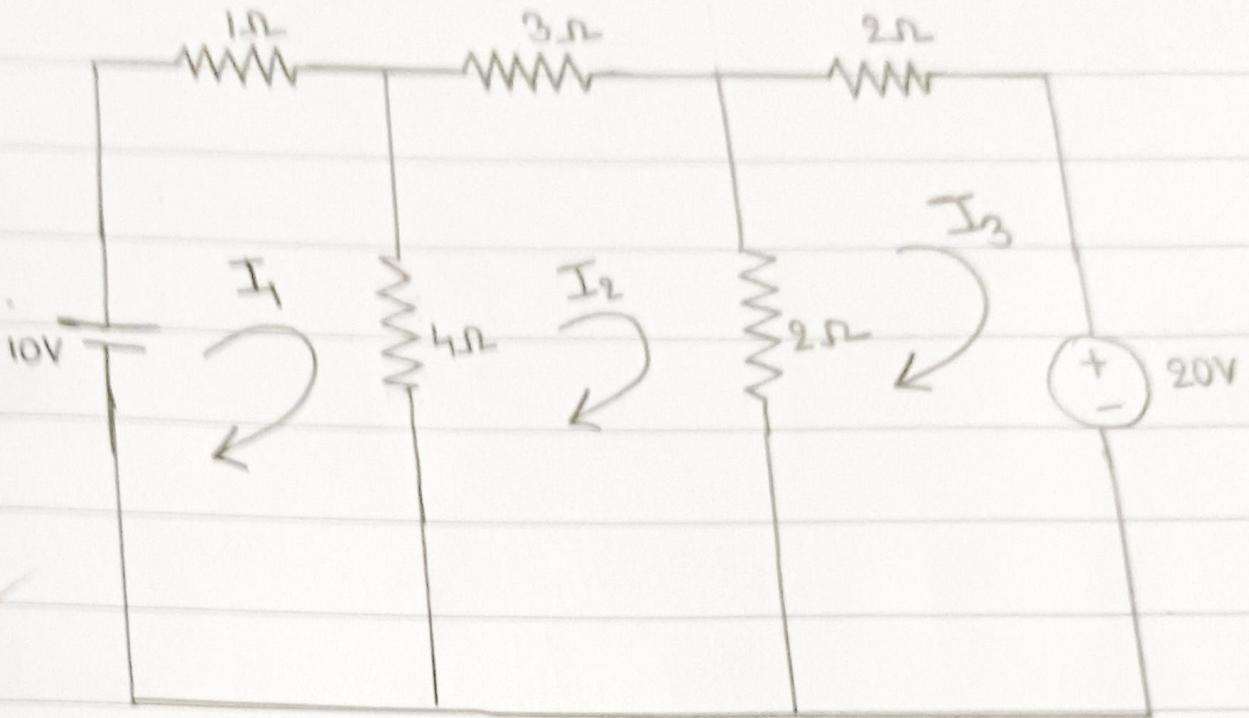

Apply Mesh analysis for loop 1

$$10 - I_1 - 4(I_1 - I_2) = 0$$

$$-5I_1 + 4I_2 = -10 \quad \textcircled{1}$$

Apply Mesh analysis for loop 2

$$-3I_2 - 2(I_2 - I_3) - 4(I_2 - I_1) = 0$$

$$4I_1 - 9I_2 + 2I_3 = 0 \quad \textcircled{2}$$

Apply Mesh analysis for loop 3

$$-2I_3 - 20 - 2(I_2 - I_3) = 0$$

$$2I_2 - 4I_3 = 20 \quad \text{--- (3)}$$

By solving eq (1), (2) & (3)

$$I_1 = 1.66A$$

$$I_2 = 0.416A$$

$$I_3 = -2.21A$$

Compassion Table :-

No	Parameter	Theoretical	Practical
1.	I_1	1.66A	1.66A
2.	I_2	-0.416A	-0.416A
3.	I_3	-2.21A	-2.21A

Result:-

Hence Mesh analysis is verified both theoretically as well as using simulation tools.

21/12/2021

Experiment - 6

P.No 95

Verification of nodal analysis

Aim:-

To simulate the given circuit using MATLAB Simulink and verify nodal analysis

Apparatus Required:


1. Laptop / Desktop
2. MATLAB

Requirements:

Components	Tool Box library browser	Block	Parameters
Voltage Source	Simpower System/ Electrical Sources	DC Voltage Source	Amplitude = 50V, 40V
Resistors	Simpower system/ Elements	Series RLC branch (Select R)	Resistance = 10, 40, 12, 30 Ω 20
Measurements	Simpower System/ electrical measurements	Current/ Voltage Measurement	Default
Display Powergui	Simulink / Sims Simpower System/ Elements	Display Powergui	Default Continuous

Steps to do Nodal Analysis:-

Theoretical Calculations:-

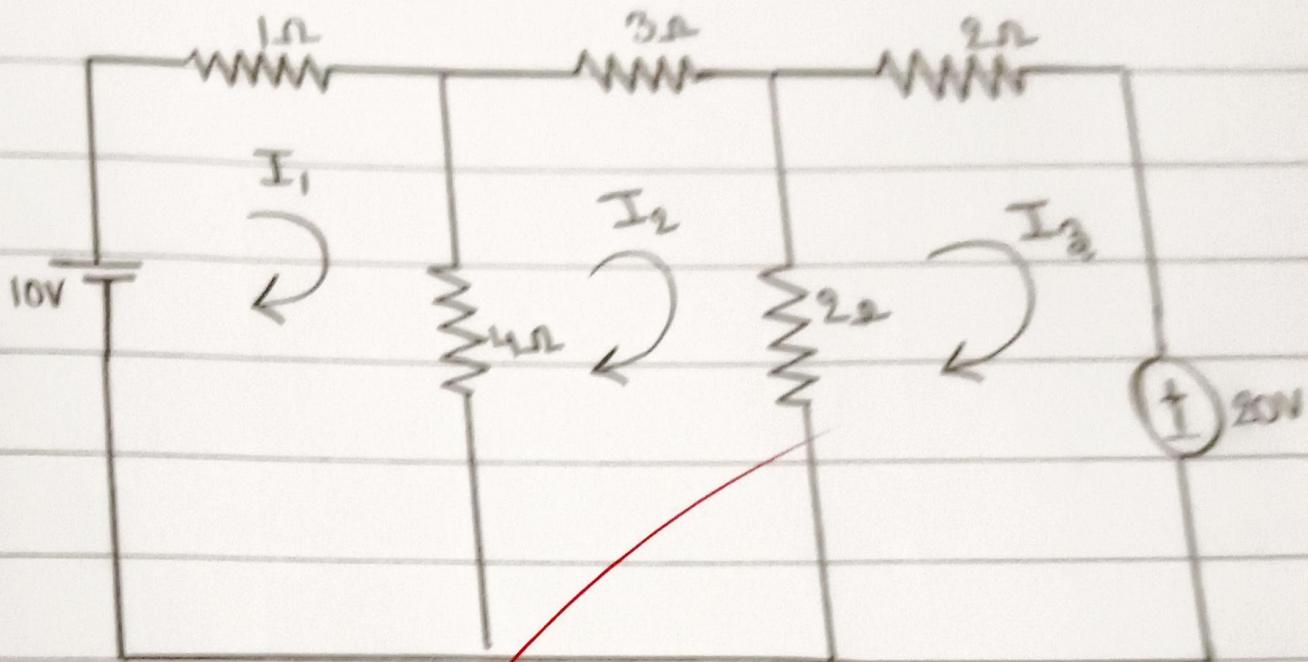

Apply Nodal analysis at loop 1

$$\frac{V_1 - 10}{1} + \frac{V_1}{4} + \frac{V_1 - V_2}{3} = 0$$

$$19V_1 - 120 + 3V_1 + 4V_1 - 4V_2 = 0$$

$$19V_1 - 4V_2 - 120 = 0 \quad \text{--- (1)}$$

Apply Nodal analysis at Loop ②

$$\frac{V_2 - V_1}{\frac{1}{2}} + \frac{V_2}{2} + \frac{V_2 - 20}{2} = 0$$

$$2V_2 - 2V_1 + 3V_2 + 3V_2 - 60 = 0$$

$$-2V_1 + 8V_2 - 60 = 0 \quad \textcircled{2}$$

By solving eq ① & ②
we get

$$V_1 = 8.33V$$

$$V_2 = 9.58V$$

Current passing through 1Ω resistor

$$I = \frac{10 - V_1}{1} = \frac{10 - 8.33}{1}$$

$$\boxed{I = 1.67A}$$

Comparison Table :-

S.NO	Parameters	Theoretical	Practical
1.	V_1	8.33V	8.33V
2.	V_2	9.58V	9.58V
3.	$I_{1\Omega}$	1.67A	1.67A

Result:-

Hence Nodal analysis is verified both theoretically as well as using simulation tools.

AM
31/12/2019

Experiment - 7

P.No 28

Generation of various signals like impulse signal/
impulse wave form step signal, square waveform, sinusoidal
signal, ramp, triangular signal.

Aim: To generate various signals & sequences (Periodic & Aperiodic)
such as unit Impulse, Step, Square, Sawtooth, Triangular,
Sinusoidal, Ramp using MATLAB Simulink.

Apparatus Required:-

1. Laptop / Desktop
2. MATLAB

Generation of Sawtooth wave form:-

clc;

clear all;

close all;

$t = 0 : 0.001 : 0.1$

$$y_2 = t$$

$$y = 10 * \text{Sawtooth}(2 * \pi * 50 * t)$$

plot(t, y)

Generation of Square wave form:-

clc;

clear all;


close all;

$t = 0 : 0.001 : 0.1$

$y_2 = t$

$y = 10 * \text{square}(2 * \pi * 50 * t)$

plot(t, y)

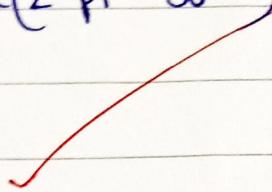

Generation of Sinusoidal wave form:-

dc;

clear all;

close all;

t = 0:0.1:2

for i = 1:length(t)

if ($0 \leq t(i) \leq 1$)

$$x(:, i) = \sin(\pi * t(i))$$

elseif ($1 < t(i) \leq 2$)

$$x(:, i) = -2 * \sin(\pi * t(i))$$


else

$$x(:, i) = 0$$

end

end

plot (t, x)

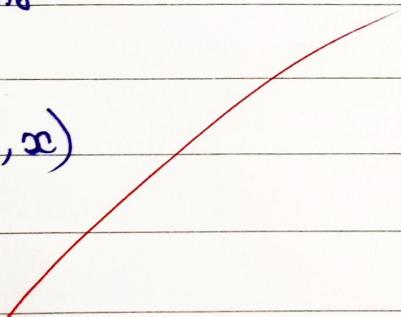

Generation of Unit Impulse Waveforms:-

clc;

clear all;

close all;

$t_1 = -1 : 0.01 : 1$

for i = 1 : length(t_1)

$t_1 = -1 : 0.01 : 1$

if $t_1(i) < 0$

$y_1(:, i) = 0$

elseif $t_1(i) = 0$

$y_1(:, i) = 1$

else

$y_1(:, i) = 0$

end

end

plot(t_1, y_1);

xlabel('time');

ylabel('amplitude');

title('Unit impulse signal');

Generation of unit step wave form:-

clc;

clear all;

close all;

$t_2 = -10 : 0.2 : 10;$

for i = 1 : length(t_2)

if $t_2(i) < 0$

$y_1(:, i) = 0;$

elseif $t_2 = 0$

$y_1(:, i) = 1;$

else

$y_1(:, i) = 1;$

end

end

~~$y_2 = (t_2 \geq 0);$~~

~~plot(t_2, y_2);~~

~~x label('time');~~

~~y label('amplitude');~~

~~title('Unit Step Signal');~~

Generation of triangular waveform.

dt =

clear all;

close all;

t = 0:0.001:0.1;

T₀ = t;


$$y = 10 * \sin(2 * \pi * 50 * \frac{t}{T_0}, 0.5)$$

plot(t, y)

xlabel('Time');

ylabel('Amplitude');

title('Triangular Signal');

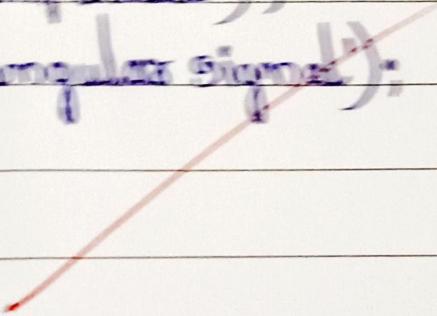

Generation of Ramp signal waveform:-

dc;

clear all;

close all;

t = 0: 0.001: 0.1;

y₂ = t;

plot(t, y₂)

x label('time');

y label('amplitude');

title('Ramp Signal');

Result:-

Hence generation of various Signals & Sequences
Such as Unit Impulse, Step, Square, Saw tooth,
Triangular, Sinusoidal, Ramp are verified using
Simulink tools.

Dr
01/01/2022

Experiment 8

P No 35

Operations on signals & sequences such as Addition, Multiplication, Scaling, Shifting, Folding, Computation of Energy, and Average Power.

Aim: To operate signals and sequences such as Addition, Multiplication, Scaling, Shifting, Folding, Computation of Energy, and Average Power using MATLAB simulink.

Apparatus Required:-

- 1. Laptop/Desktop
- 2. MATLAB

Addition of two Signals:-

% generating two input signals

clc;

clear all;

close all;

t = 0:0.1:1;

$x_1 = \sin(2 * \pi * 4 * t);$

$x_2 = \sin(2 * \pi * 8 * t);$

subplot (2, 2, 1);

plot (t, x1);

x label ('time');

y label ('amplitude');

title ('input signal 1');

subplot (2, 2, 2);

plot (t, x2);

x label ('time');

y label ('amplitude');

title ('input signal 2');

% addition of signals

$y_1 = x_1 + x_2;$

subplot (2, 2, 3);

plot (t, y1);

x label ('time');

y label ('amplitude');

title ('addition of two signals');

Multiplication of two signals:-

% generating two input signals

clc;

clear all;

clear all;

t = 0:0.1:1;

$x_1 = \sin(2 * \pi * 4 * t);$

$x_2 = \sin(2 * \pi * 8 * t);$

subplot(2,2,1);

plot(t, x1);

x label('time');

y label('amplitude');

title('input signal 1');

subplot(2,2,2);

plot(t, x2);

x label('time');

y label('amplitude');

title('input signal 2');

% multiplication of signals

$y_2 = x_1 * x_2;$

subplot(2,2,3);

plot(t, y2);

x label('time');

y label('amplitude');

title('multiplication of two signals');

Scaling of a signal:-

% generating two input signals

dc;

clear all;

close all;

t = 0:0.1:1;

$$x_1 = \sin(2 * \pi * 4 * t);$$

$$x_2 = \sin(2 * \pi * 8 * t);$$

% Scaling of a signal 1

A = 15;

$$y_3 = A * x_1;$$

figure;

subplot(2,2,1);

plot(t, x1);

xlabel('time');

ylabel('amplitude');

title('input signal');

subplot(2,2,2);

plot(t, y3);

xlabel('time');

ylabel('amplitude');

title('amplified input signal');

Shifting of a Signal:-

% generating two input signals

dc;

clear all;

close all;

t = 0:0.1:1;

x₁ = sin(2 * pi * 4 * t);

figure;

subplot(2,1,1);

plot(t, x₁);

subplot(2,1,2);

plot(t + 2, x₁);

xlabel('t + 2');

ylabel('amplitude');

title('right shifted signal');

Result:-

Hence operations on Signals & Sequences such as Addition, Multiplication, Scaling, Shifting, Folding, Computation of energy & Average power are verified using Simulation tools.

AM

28/01/2022

Experiment-9

P.No 40

Verification of Series Resonance Using simulation tools

Aim: To obtain the plot of frequency $V_s \cdot X_1$, frequency $V_s \cdot X_C$, frequency $V_s \cdot$ impedance and frequency $V_s \cdot$ Current for the given series RLC Circuit and determine the resonant frequency & check by theoretical calculations. $R = 15 \Omega$, $C = 10 \mu F$, $L = 0.1 H$, $V = 50V$ vary frequency in steps of 1Hz Using Matlab.

% Program to find the Series Resonance

clc;

clear all;

close all;

$r = \text{input}(\text{'enter the resistance value } \rightarrow \text{'});$

$L = \text{input}(\text{'enter the inductance value } \rightarrow \text{'});$

$c = \text{input}(\text{'enter the capacitance value } \rightarrow \text{'});$

$v = \text{input}(\text{'enter the input voltage } \rightarrow \text{'});$

$f = 5:2:300;$

$X_L = 2 * \pi * f * L;$

$X_C = (1 / (2 * \pi * f * c));$

$X = X_L - X_C$

~~$Z = \sqrt{(X^2) + (X_C^2)};$~~

$i = V / Z;$

$\text{Subplot}(2, 2, 1);$

$\text{plot}(f, X_L);$

$\text{grid};$

$\text{xlabel}(\text{'frequency'});$

$\text{ylabel}(\text{'X_L'});$

```
subplot(2,2,2);  
plot(f, xc);  
grid;  
xlabel('frequency');  
ylabel('xc');  
subplot(2,2,3);  
plot(f, z);  
grid;  
xlabel('frequency');  
ylabel('z');  
subplot(2,2,4);  
plot(f, i);  
grid;  
xlabel('frequency');  
ylabel('I');
```

Result:- Hence Series resonance is verified using simulation tools.

✓
25/01/2022

Experiment - 10

Verification of Parallel Resonance using Simulation tools

P.No 72

Aim:- To obtain the graphs of frequency vs. BL , frequency vs. BC , frequency vs. admittance & frequency vs. current vary frequency in steps for the given circuit & find the resonant frequency & check by theoretical calculations. $R = 1000 \Omega$, $C = 400 \mu\text{F}$, $L = 1\text{H}$, $V = 50\text{V}$ vary frequency in steps of 1Hz using Matlab.

% Program to find the Parallel Resonance
dc;

clear all;

close all;

~~$r = \text{input}('enter the resistance value \rightarrow');$~~

~~$L = \text{input}('enter the inductance value \rightarrow');$~~

~~$C = \text{input}('enter the capacitance value \rightarrow');$~~

~~$V = \text{input}('enter the input voltage \rightarrow');$~~

$f = 0:2:50;$

$$XL = 2 * \pi * f * L;$$

$$XC = (1 / (2 * \pi * f * C));$$

$$BL = 1 / XL;$$

$$BC = 1 / XC;$$

$$b = BL - BC;$$

$$g = 1 / \sigma;$$

$$\gamma = \text{sqrt}((g^2) + (b \cdot \sigma^2));$$

```
i=v*y; % plotting the graph  
subplot(2,2,1);  
plot(f,b1);  
grid;  
xlabel('frequency');  
ylabel('B1');  
subplot(2,2,2);  
plot(f,bc);  
grid;  
xlabel('frequency');  
ylabel('Bc');  
subplot(2,2,3);  
plot(f,y);  
grid;  
 xlabel('frequency');  
y label('y');  
subplot(2,2,4);  
plot(f,i);  
grid;  
 xlabel('frequency');  
y label('I');
```

29/01/2012

Theory - Result:-

Hence parallel resonance is verified using simulation tools.